

# Chapter 6

## **Chapter 6 The Usage of LPM Macro Module**

# IP



## ⌘ Intel PSG

- ☑ MegaCore

- ☑ LPM

⌘ The macro modules and LPM functions of Quartus II include:

- ☒ Arithmetic component: adder, multiplier, accumulator, etc.
- ☒ Combinational circuit: multiplexer, comparer, LPM gate function, etc.
- ☒ I/O component: PLL, etc.
- ☒ Memory: FIFO、RAM、ROM, etc.
- ☒ IP of single-chip computer, etc.

# The Example of Invoking Macro Module of Counter

⌘ This section gives the general usage methods of MegaWizard Plug-In Manager for the same type of macro modules by introducing the process of invoking and testing the LPM counter LPM\_COUNTER.

# The Invoking of the Text Code of the Counter LPM Module

## Open the MegaWizard Plug-In Manager



Figure: Customizing new macro function block

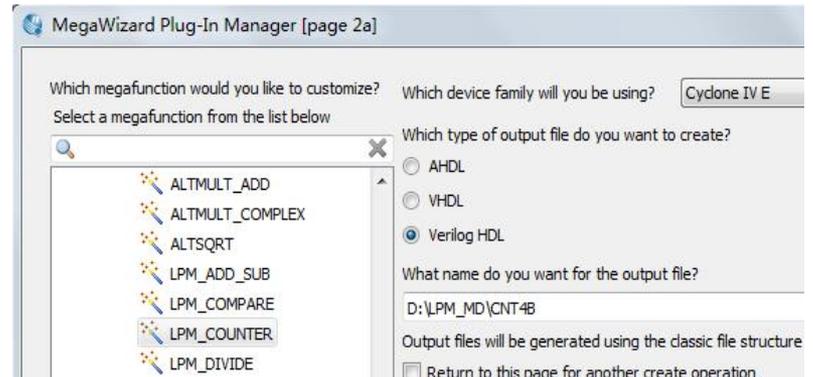


Figure: Setting the LPM macro function block

Set up the project folder, for example, d:\LPM\_MD, and choose Tools->MegaWizard Plug-In Manager.

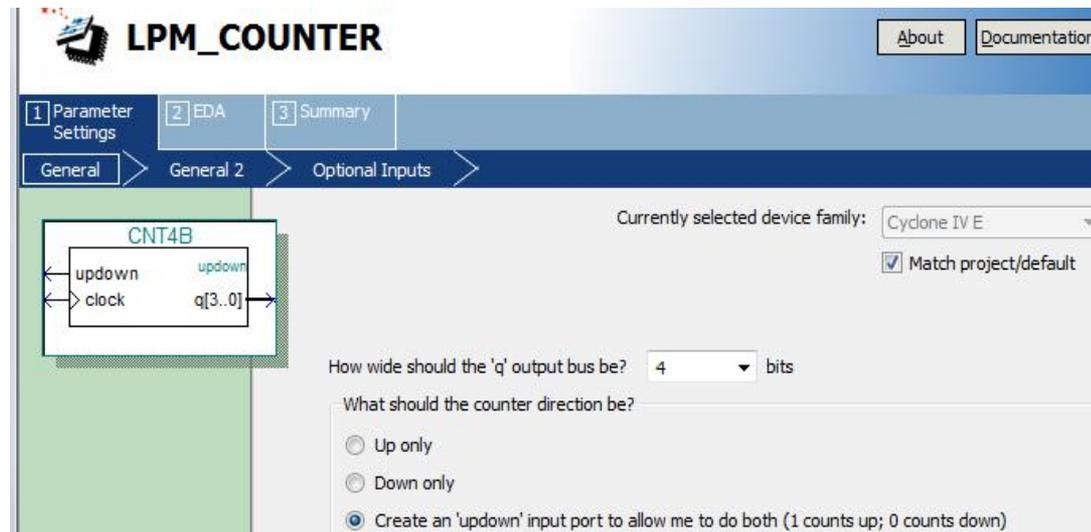


Figure: The setting of 4-bit counter with addition and subtraction

Choose 4-bit counter and

choose “Create an updown input...”, which makes the counter have the control functionality of add/subtract.

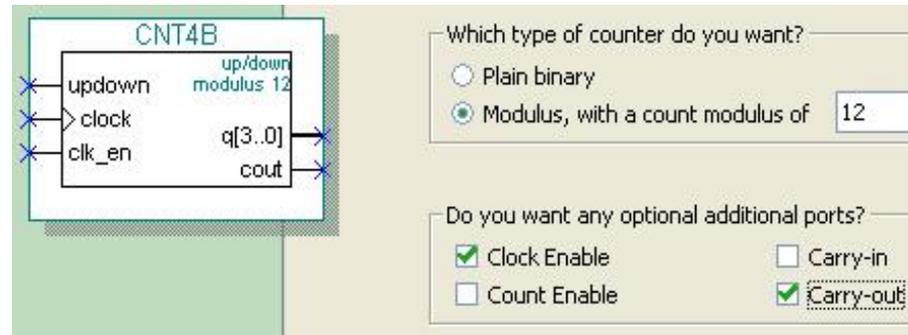



Figure: Setting the counter with the clock enable and carry output

Plain binary: common binary counter

Modulus...: counter with the modulus of ...

Clock Enable: clock enable control

Carry-out: carry-out

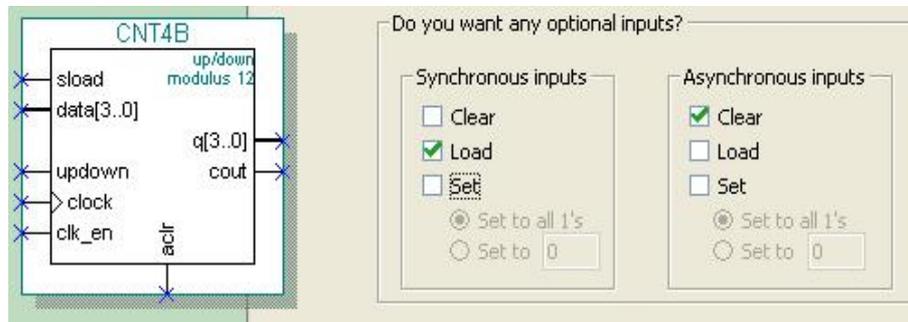

Choose synchronous load and asynchronous clear

Figure: Adding 4-bit parallel data preset functions

The above-mentioned processes generate the Verilog file of the LPM counter, named "CNT4B.v", which can be invoked by the higher level Verilog program as the counter component.

## 6.1.2 Application of LPM Counter Code and Parameter Transmission Statement

```

⌘ [Example]
⌘ module CNT4B (aclr, clk_en, clock, data, sload, updown, cout, q);
⌘     input aclr, clk_en;           //asynchronous clear,1 clear; clock enable, 1 enable, 0 disable
⌘     input clock, sload;         //clock input; synchronous preset load control, 1 load, 0 count
⌘     input [3:0] data; input  updown; //4-bit preset number, and addition and subtraction control, 1 addition, 0 subtraction
⌘     output cout; output [3:0] q; //carry output and 4-bit count output
⌘     wire sub_wire0; wire [3:0] sub_wire1; // Defining internal connections
⌘     wire cout = sub_wire0; // The same assignment statement as assign
⌘     wire [3:0] q = sub_wire1[3:0]; // The same assignment statement as assign
⌘     lpm_counter lpm_counter_component( // Note that the unused ports in the instantiated statement must be connected to
the specified level.
⌘         .sload(sload), .clk_en(clk_en), .aclr(aclr),
⌘         .data(data), .clock(clock), .updown(updown),
⌘         .cout(sub_wire0), .q(sub_wire1), .aload(1'b0),
⌘         .aset(1'b0), .cin(1'b1), .cnt_en(1'b1),
⌘         .eq(), .sclr(1'b0), .sset(1'b0));
⌘     defparam
⌘         lpm_counter_component.lpm_direction = "UNUSED", // Unused unidirectional counting parameters
⌘         lpm_counter_component.lpm_modulus = 12, //counter with modulus of 12
⌘         lpm_counter_component.lpm_port_updown = "PORT_USED", // Use the addition and subtraction count
⌘         lpm_counter_component.lpm_type = "LPM_COUNTER", // Counter type
⌘         lpm_counter_component.lpm_width = 4; // Counting bit width
⌘ endmodule

```

- ⌘ The general description of the parameter transmission statement *defparam* is given as follows:
- ⌘ `defparam < macro module component instantiation name >.  
< macro module parameter name > = < parameter value >`

### [ Example ]

```
module REG24B (d, clk, q);
    input [23:0] d;    input  clk;
    output [23:0] q;
    lpm_ff U1(.q (q[11:0]), .data (d[11:0]), .clock (clk));
        defparam U1.lpm_width = 12;
    lpm_ff U2(.q(q[23:12]), .data(d[23:12]), .clock(clk));
        defparam U2.lpm_width = 12;
endmodule
```

For invoking the counter file "CNT4B.v" , testing and implementing the counter, a program must be designed to instantiate it. Example of 6-3 is used to realize the functionality.

### [ Example ]

```
module CNT4BIT (RST,ENA,CLK,DIN,SLD,UD,COUT,DOUT);
    input RST, ENA, CLK, SLD,UD ;
    input [3:0] DIN;
    output COUT;    output [3:0] DOUT ;
    CNT4B U1(.sload (SLD), .clk_en (ENA), .aclr (RST), .cout (COUT),
            .clock (CLK), .data (DIN), .updown (UD), .q (DOUT));
endmodule
```

# 6.1.3 Project Creation and Simulation Testing

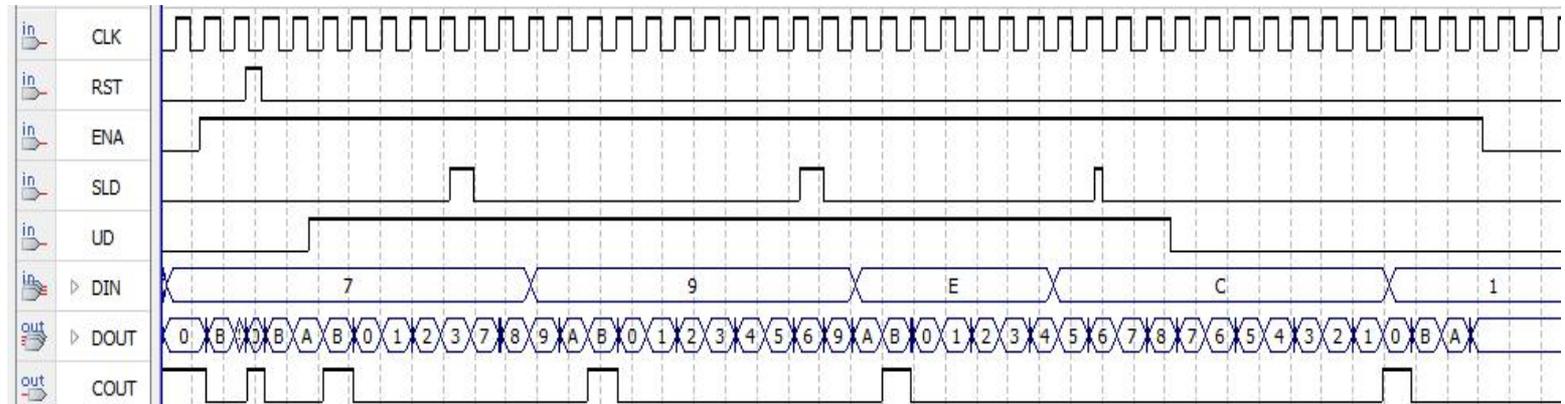


Figure: The simulation waveform of CNT4BIT.v

## 6.2 Example of Building Attribute Control Multiplier

For implementing the multiplier, if use conventional method, the synthesized multiplier will occupy large logic resource and the speed may not be high. The useful method is to invoke the embedded hardware multiplier in the FPGA and this type of multiplier is commonly used in DSP technology. Thus, this type of multiplier is called DSP module.

`/* synthesis multstyle = "logic" */` The way of pure combinational logic  
`/* synthesis multstyle = "dsp" */` The way of invoking FPGA embedded multiplier

### [ Example ]

```

module MULT8 (A1,B1,A2,B2,R1,R2) ;
    output signed[15:0] R1, R2 ;           // Defining the output of the signed data
                                         //type
    input signed[7:0] A1,B1,A2,B2;       // Defining the input of the signed data
                                         //type

    wire [15:0] R2, R1 ;
    assign R1 = A1 * B1 ;    assign R2 = A2 * B2 ;

endmodule

```

The multiplier which uses R2 as the output port is constructed by the macro unit utilizing the way of pure combinational logic.

The multiplier which uses R1 as the output port is constructed by invoking the embedded multiplier in FPGA.



```
⌘ wire [15:0] R2 /* synthesis multstyle = "logic" */
```

```
⌘ wire [15:0] R2, R1 /* synthesis multstyle = " logic " */
```

If the multiplier in the overall module is required to be constructed by using DSP module, the program can be written as follows:

```
⌘ module andd(A1,B1,A2,B2,R1,R2) /* synthesis multstyle = "dsp" */;
```

Flow Status	Successful - Tue May 23 21:32:59 2017
Quartus II 64-Bit Version	13.1.0 Build 162 10/23/2013 SJ Full Version
Revision Name	MULT8
Top-level Entity Name	MULT8
Family	Cyclone IV E
Device	EP4CE55F23C8
Timing Models	Final
Total logic elements	190 / 55,856 ( < 1 % )
Total combinational functions	190 / 55,856 ( < 1 % )
Dedicated logic registers	0 / 55,856 ( 0 % )
Total registers	0
Total pins	64 / 325 ( 20 % )
Total virtual pins	0
Total memory bits	0 / 2,396,160 ( 0 % )
Embedded Multiplier 9-bit elements	0 / 308 ( 0 % )
Total PLLs	0 / 4 ( 0 % )

Figure: The compilation report of completely using logic macro units to construct the multiplier

Flow Status	Successful - Tue May 23 21:30:42 2017
Quartus II 64-Bit Version	13.1.0 Build 162 10/23/2013 SJ Full Version
Revision Name	MULT8
Top-level Entity Name	MULT8
Family	Cyclone IV E
Device	EP4CE55F23C8
Timing Models	Final
Total logic elements	0 / 55,856 ( 0 % )
Total combinational functions	0 / 55,856 ( 0 % )
Dedicated logic registers	0 / 55,856 ( 0 % )
Total registers	0
Total pins	64 / 325 ( 20 % )
Total virtual pins	0
Total memory bits	0 / 2,396,160 ( 0 % )
Embedded Multiplier 9-bit elements	2 / 308 ( < 1 % )
Total PLLs	0 / 4 ( 0 % )

Figure: The compilation report of invoking DSP module

## The compiling report of example 6-4

Flow Status	Successful - Tue May 23 21:32:59 2017
Quartus II 64-Bit Version	13.1.0 Build 162 10/23/2013 SJ Full Version
Revision Name	MULT8
Top-level Entity Name	MULT8
Family	Cyclone IV E
Device	EP4CE55F23C8
Timing Models	Final
Total logic elements	190 / 55,856 ( < 1 % )
Total combinational functions	190 / 55,856 ( < 1 % )
Dedicated logic registers	0 / 55,856 ( 0 % )
Total registers	0
Total pins	64 / 325 ( 20 % )
Total virtual pins	0
Total memory bits	0 / 2,396,160 ( 0 % )
Embedded Multiplier 9-bit elements	0 / 308 ( 0 % )
Total PLLs	0 / 4 ( 0 % )

If the multiplier in the overall module is required to be constructed by using DSP module, the program can be written as follows:

```
module andd(A1,B1,A2,B2,R1,R2) /* synthesis multstyle = "dsp" */;
```

Flow Status	Successful - Tue May 23 21:30:42 2017
Quartus II 64-Bit Version	13.1.0 Build 162 10/23/2013 SJ Full Version
Revision Name	MULT8
Top-level Entity Name	MULT8
Family	Cyclone IV E
Device	EP4CE55F23C8
Timing Models	Final
Total logic elements	0 / 55,856 ( 0 % )
Total combinational functions	0 / 55,856 ( 0 % )
Dedicated logic registers	0 / 55,856 ( 0 % )
Total registers	0
Total pins	64 / 325 ( 20 % )
Total virtual pins	0
Total memory bits	0 / 2,396,160 ( 0 % )
Embedded Multiplier 9-bit elements	2 / 308 ( < 1 % )
Total PLLs	0 / 4 ( 0 % )

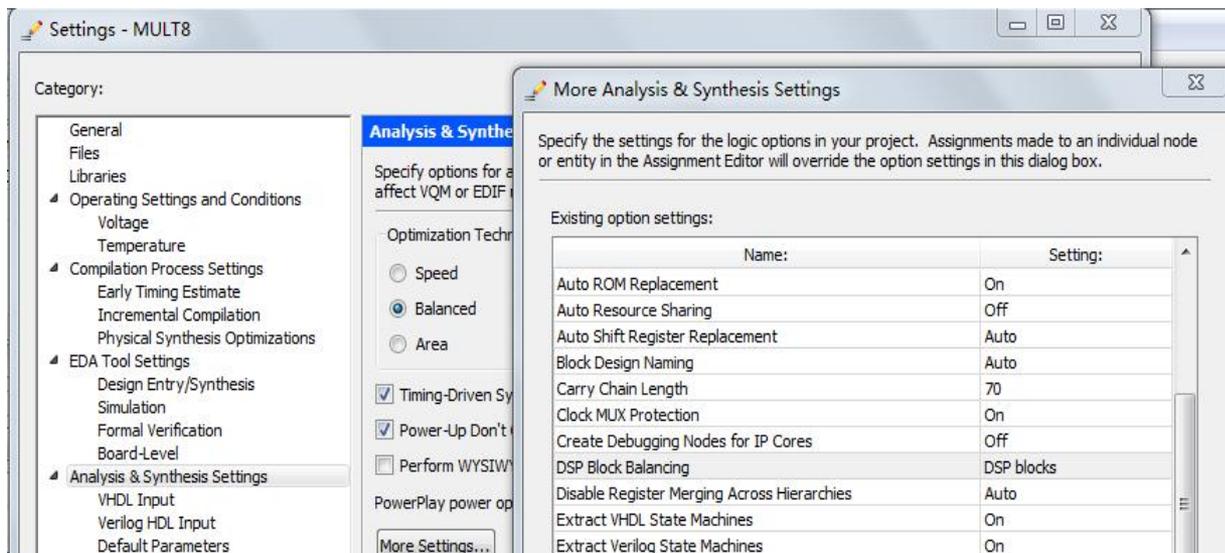


Figure: Selecting DSP Block Balancing as DSP blocks

# 6.3 Usage of Macro Block of LPM\_RAM

- ⌘ In the design and development of involving memory applications such as RAM and ROM, invoking LPM module-type memory is the most convenient, most economical, most effective, and most efficient way to satisfy the design requirements. The following introduces the related technologies of using Quartus II to invoke LPM\_RAM, including simulation test, generation of initialization configuration file, instantiation program expression, related attribute application and Verilog language description of memory.


# 6.3.1 Initialization File and Its Generation

- ⌘ In the design and development of the RAM and ROM applications, invoking LPM memory is the most convenient and cost-effective way for satisfying the design requirements.
- ⌘ The initialization file of the memory is the data or code that can be configured in RAM or ROM. In the EDA design, the memory code file set or designed by the EDA tools is automatically invoked in the unified compilation.
- ⌘ Quartus II can accept two types of initialization files: .mif and .hex.

# ⌘ 1. .mif format file
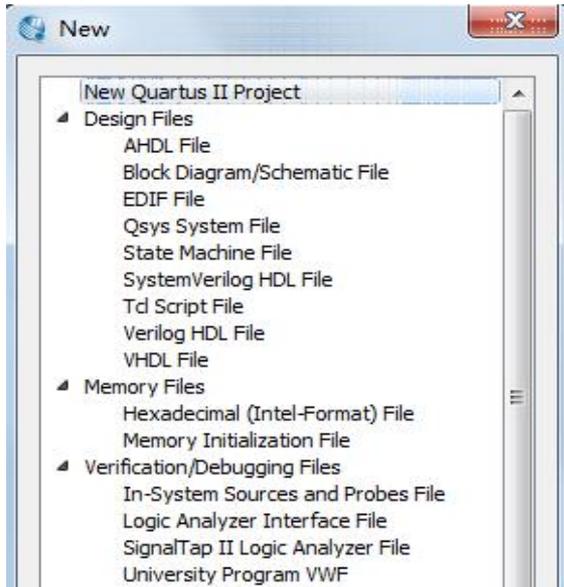
## (1) The method of direct editing

File -> New -> Memory Initialization File



DATA7X8.mif								
Addr	+0	+1	+2	+3	+4	+5	+6	+7
00	80	86	8C	92	98	9E	A5	AA
08	B0	B6	BC	C1	C6	CB	D0	D5
10	DA	DE	E2	E6	EA	ED	F0	F3
18	F5	F8	FA	FB	FD	FE	FE	FF
20	FF	FF	FE	FE	FD	FB	FA	F8
28	F5	F3	F0	ED	EA	E6	E2	DE
30	DA	D5	D0	CB	C6	C1	BC	B6
38	B0	AA	A5	9E	98	92	8C	86
40	7F	79	73	6D	67	61	5A	55
48	4F	49	43	3E	39	34	2F	2A
50	25	21	1D	19	15	12	0F	0C
58	0A	07	05	04	02	01	01	00
60	00	00	01	01	02	04	05	07
68	0A	0C	0F	12	15	19	1D	21
70	25	2A	2F	34	39	3E	43	49
78	4F	55	5A	61	67	6D	73	79

## 1. .mif format

### (2) The method of file editing

Example:


```
DEPTH=128;   The number of data in memory
WIDTH=8;     Width of output data
ADDRESS_RADIX = HEX;  The data type of address
DATA_RADIX = HEX;    The data type of memory
CONTENT
BEGIN
0000      :      0080;
0001      :      0086;
0002      :      008C;
...
007E      :      0073;
007F      :      0079;
END;
```

Regular editor can be used to design MIF file. Address and data are both hexadecimal.

Save as .mif file

## 1. .mif format

### (3) specific mif file generator

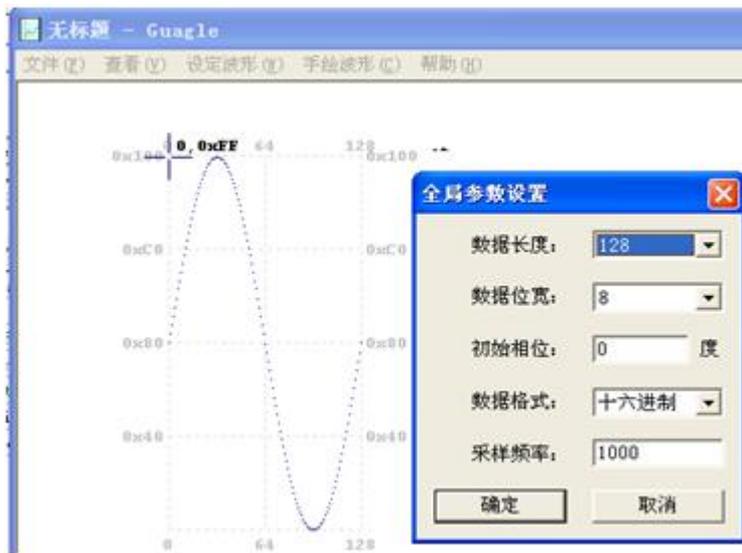

The screenshot shows a text editor window titled "DATA7X8.mif - 记事本" with a menu bar containing "文件(F)", "编辑(E)", "格式(O)", and "查". The content of the file is as follows:

```
DEPTH = 128;
WIDTH = 8;
ADDRESS_RADIX = HEX;
DATA_RADIX = HEX;
CONTENT BEGIN
0000 : 0080;
0001 : 0086;
0002 : 008C;
0003 : 0092;
0004 : 0098;
0005 : 009E;
0006 : 00A5;
0007 : 00AA;
0008 : 00B0;
...
007E : 0073;
007F : 0079;
END ;
```

Figure: Generation of .mif sinusoidal waveform file by using mif generator

Figure: Open .mif file

## 2. .hex format file

- (1) method 1: New -> Hexadecimal (Intel-Format) File -> save as .hex format file
- (2) method 2: The data is edited in HEX data editing window by using assembly program editor and .hex format file is generated by using assembly compiler.

## 3. .dat format file

.mif and .hex format file is related with the specific development software, as the invoking of them in Verilog text is necessarily required to use the stipulated property expression of Quartus II.

However, the invoking of .dat format data file can be realized directly by using standard Verilog statements. The data format of .dat file is simplest and its form is given as follows:

```
00 E5 6D ... 34
```

# 6.3.2 Invoking LPM\_RAM by Schematic Diagram Method


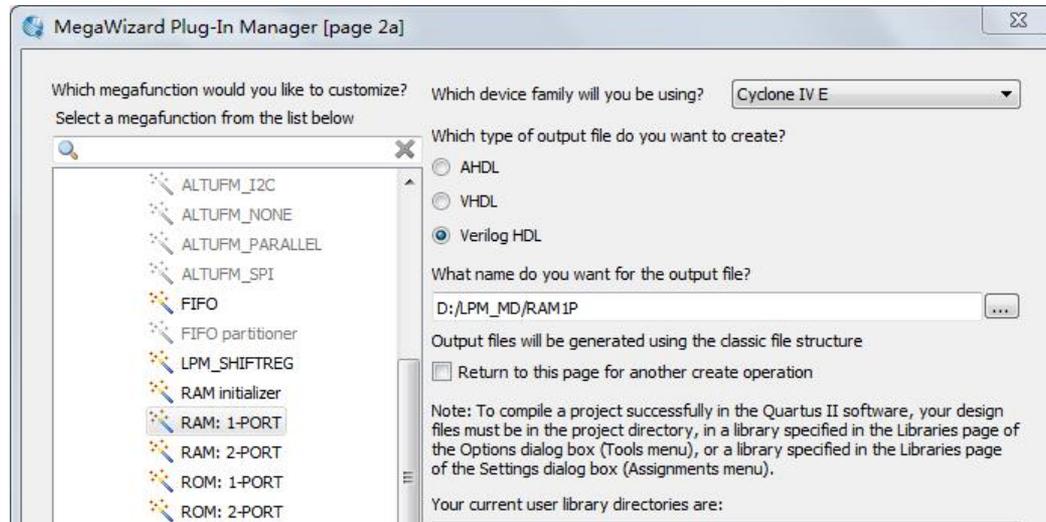


Figure: Invoking single port LPM RAM

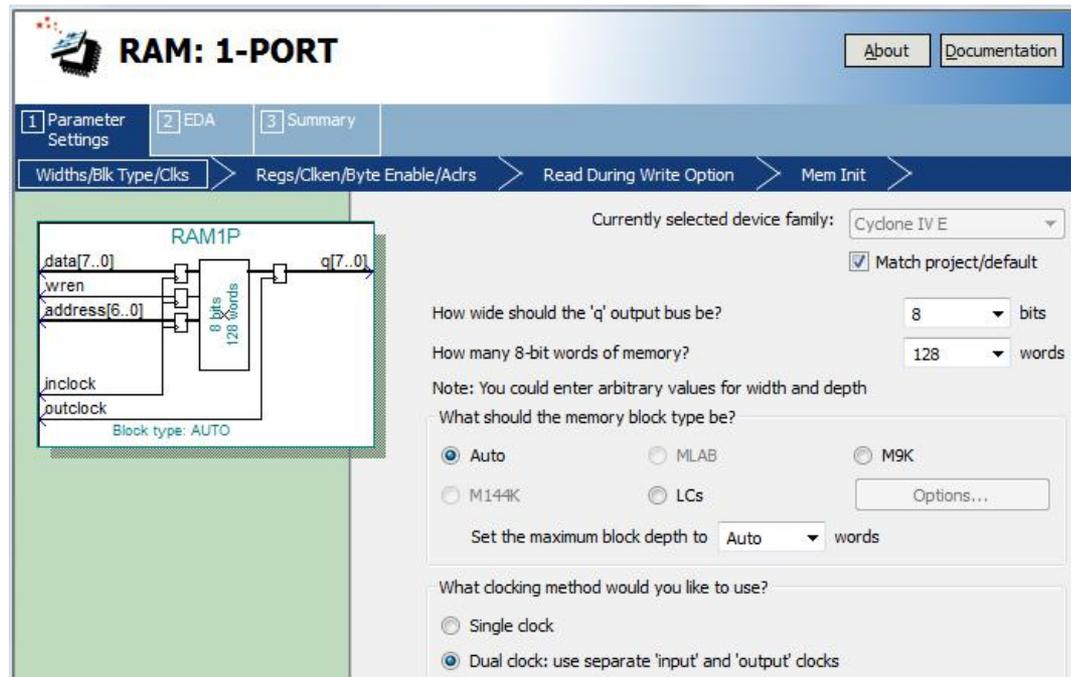

**RAM: 1-PORT**

Parameter Settings | EDA | Summary

Widths/Blk Type/Ckls | Regs/Ckln/Byte Enable/Adrs | Read During Write Option | Mem Init

Currently selected device family: Cyclone IV E

Match project/default

How wide should the 'q' output bus be? 8 bits

How many 8-bit words of memory? 128 words

Note: You could enter arbitrary values for width and depth

What should the memory block type be?

Auto  MLAB  M9K  
 M144K  LCs

Set the maximum block depth to Auto words

What clocking method would you like to use?

Single clock  Dual clock: use separate 'input' and 'output' clocks

Figure: Setting RAM parameters

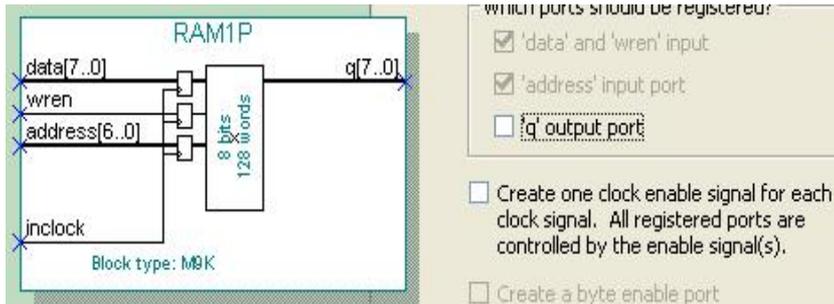


Figure: Setting RAM to be controlled by input clock only

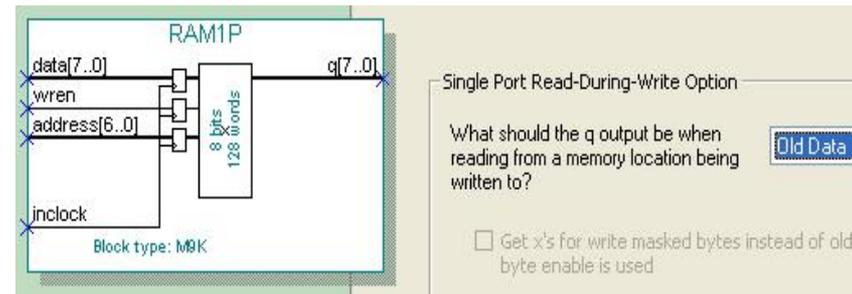


Figure: Setting to read the original data at the same time of writing data: Old Data

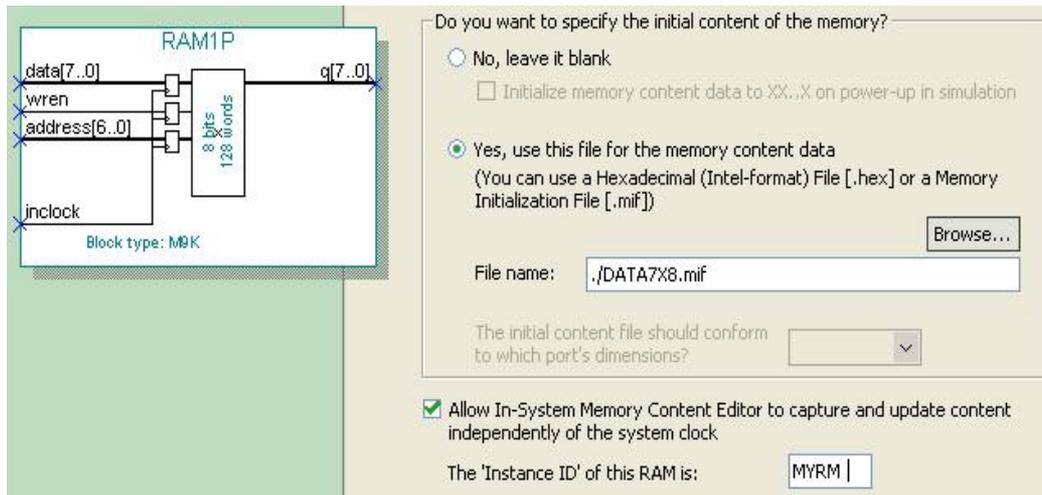


Figure: Setting the initialization file and allowing the in-system editing

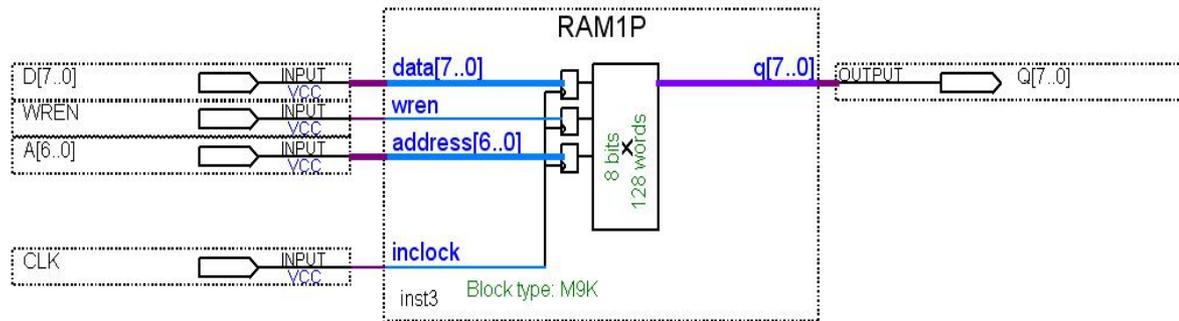


Figure: The well-connected RAM module on a schematic diagram

# 6.3.3 Test LPM\_RAM

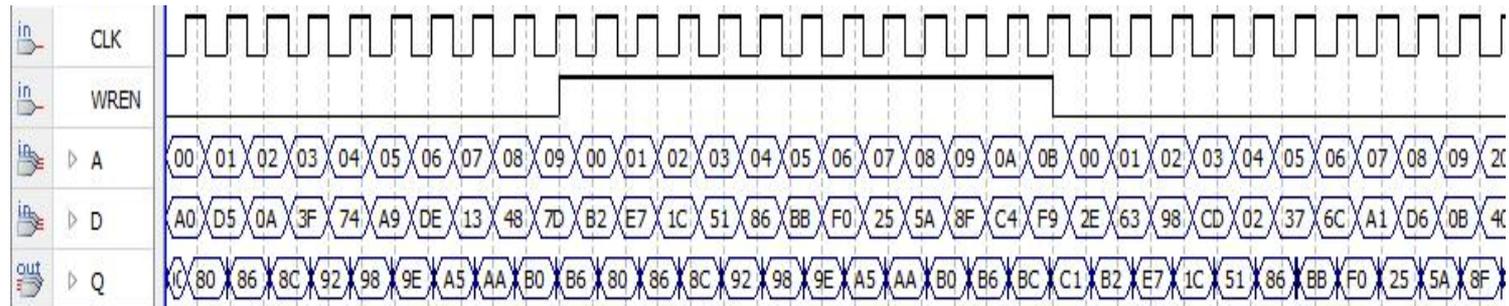


Figure: The simulation waveform of RAM

## 6.3.4 Expression of Memory Initialization File Loading of Verilog Code Description

- ⌘ In Section 6.3.2, the reader has already seen that invoking the initialization file from the edited memory can use the editor called by the LPM module to select the settings in a specific dialog box (as shown in Figure 6-17). But if you invoke the initialization file in the memory of the Verilog program of the pure code, you must use a specific instruction statement. Here are two methods.
- ⌘ The first method is to use the attribute statement given by Quartus II. These statements are used only in the Quartus II platform. On the right side of the memory definition statement of Example 2-3, there are:
- ⌘ 

```
/* synthesis ram_init_file="DATA7X8.mif" */ ;
```



⌘ The following definition expression is the Verilog-2001 version and its function is same:

⌘ `(* ram_init_file = "DATA7X8.mif" *) reg[7:0]  
mem[127:0]`

The second method is to use the Verilog language directly, that is, using procedural statement *initial* and system function *\$readmemh*. Because the standard Verilog statement is used, its expression has general characteristics, so it is not limited to EDA software environment of Quartus II. As “initial” and “\$readmemh” are used, the format of initialization file must be “.dat”.

In .dat file, the data starts from lower address bit. Therefore, in example 6-6, the memory “mem” is written as mem[0:127].

**[ Example ]**

```
module RAM78 (output[7:0]Q, input[7:0]D, input[6:0]A, input CLK, WREN);  
    reg[7:0] mem[0:127] ;  
    always @(posedge CLK ) if (WREN) mem[A] <= D;  
    assign Q = mem[A];  
    initial $readmemh("RAM78_DAT.dat", mem );  
endmodule
```

## 6.3.5 Structure Control of Memory Design

The construction of memory in different Verilog expressions will obtain memories of different structures, such as a memory built by a logical macro unit or a memory built with an embedded RAM unit. The latter has the best resource utilization rate and the most concise and high-speed memory hardware structure for FPGA with large number of RAM units.

The RAMs described by Examples 6-6 and 6-7 have the same interface and function. Now let's compare their structure. The corresponding RTL diagram to Example 6-6 is shown in Figure 6-20; the corresponding RTL diagram to Example 6-7 is shown in Figure 6-21.

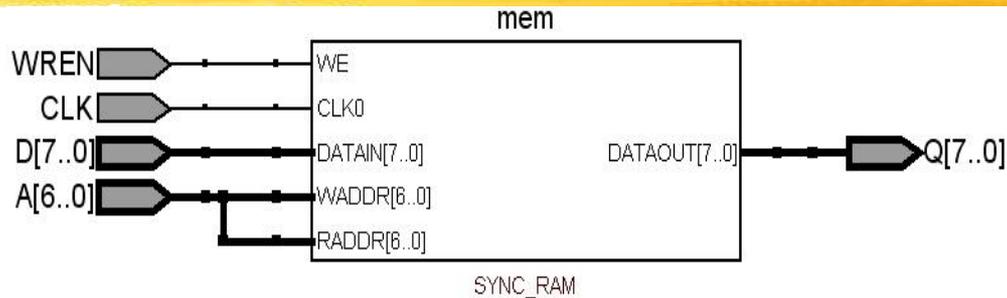


Figure: The RTL circuit module diagram of Example 6-6

**[ Example ]**

```

module RAM78(output reg[7:0] Q, input[7:0] D, input[6:0] A, input
CLK, WREN);
    reg[7:0] mem[127:0] /* synthesis ram_init_file="DATA7X8.mif" */;
    always @(posedge CLK) if (WREN) mem[A] <= D;
    always @(posedge CLK) Q = mem[A];
endmodule

```


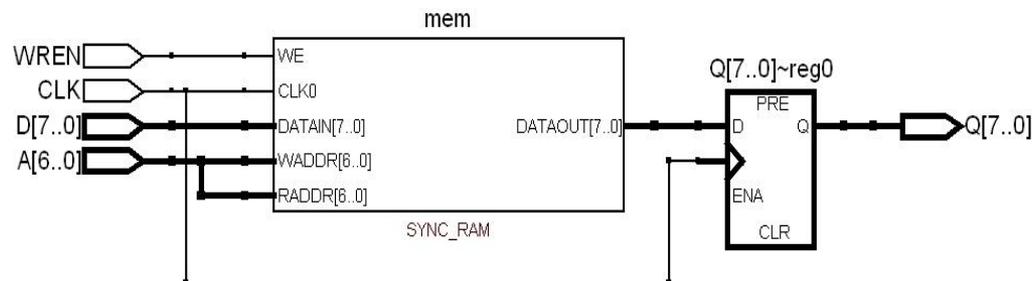


Figure: The RTL circuit module diagram of Example 6-7

- 
- ⌘ Why the differences between the example 7-6 and 7-8 are so big? The reasons are given as follows:
  - ⌘ (1) The expression way of Verilog. The output Q of the memory in Example 7-6 adopts “assign” statements. There is no any register or memory components in this case. Therefore, this structure can not use the ready-made RAM in the FPGA.
  - ⌘ Example 7-8 uses two “always” process and the output Q has an added register. This expression satisfies the RAM structure in the FPGA.

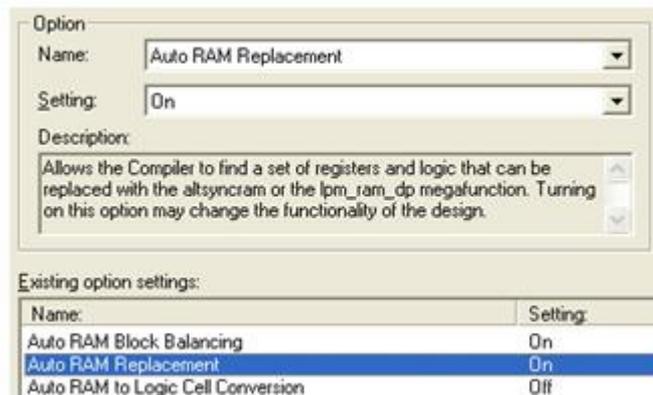(2) invoke the constraint configuration of the embedded RAM units. The correct and proper Verilog descriptions is the basis of invoking the RAM units of the FPGA, which however can not guarantee that the design will invoke the RAM units. This is because the synthesizer still does not know the design purpose of the users. For constructing the circuit with the use of RAM after synthesis, the constraint configurations are needed for the synthesizer of EDA tools.



Settings->Analysis & Synthesis  
Settings->More Settings-  
>Auto RAM Replacement->On

# 6.4 Usage Examples of LPM\_ROM

## 6.4.1 Design of Simple Sinusoidal Signal Generator

MegaWizard Plug-In Manager  
-> Memory Compiler ->  
ROM:1-PORT

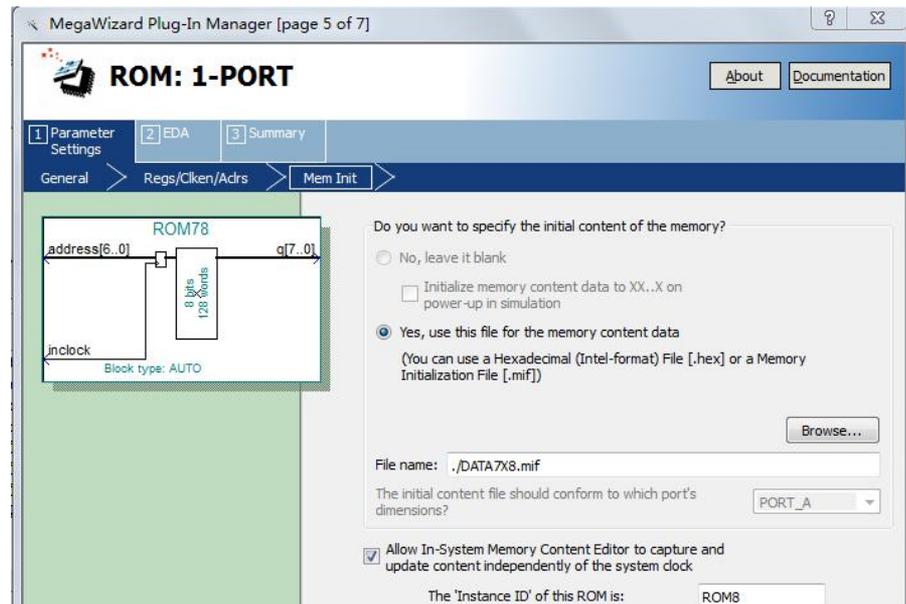


Figure: Adding the initialization configuration file and allowing in-system access to ROM content.

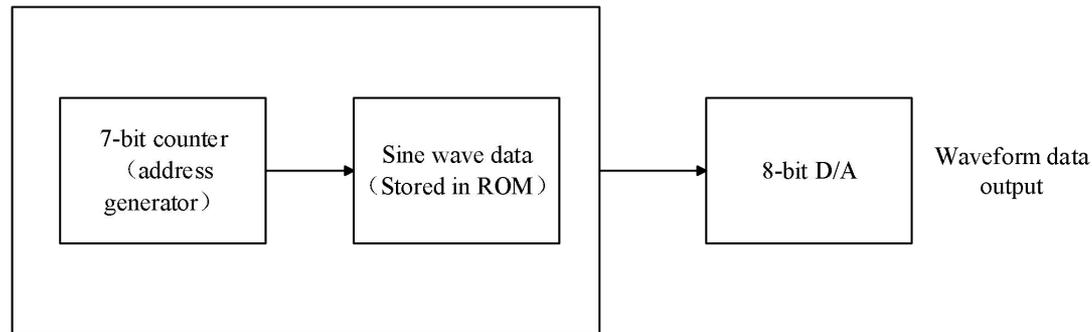


Figure: The block diagram of sinusoidal signal generator

- Counter or address signal generator. Here according to the parameters of ROM above, we select 7-bit output.
- Sinusoidal signal data memory ROM (7-bit address line, 8-bit data line), containing 128 8-bit waveform data (a sinusoidal period), that is, LPM\_ROM: ROM78.
- Design of top-level schematic diagram.
- 8-bit D/A (set the experimental device to be DAC0832 for this example).

```
module SIN_GNT(RST,CLK,EN, Q,AR);
  output [7:0] Q ; output [6:0] AR ;
  input EN,CLK,RST ; wire [6:0] TMP; reg [6:0] Q1 ;
  always @(posedge CLK or negedge RST )
    if(!RST) Q1 <=7'B0000000;
    else if (EN) Q1 <= Q1+1 ;
    else Q1 <= Q1;
  assign TMP=Q1; assign AR=TMP;
  ROM78 IC1(.address(TMP), .inclock(CLK), .q (Q) );
endmodule
```

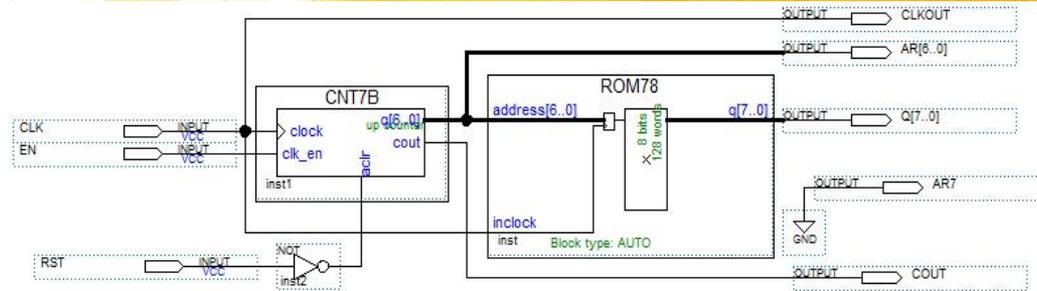


Figure: The circuit schematic diagram of sinusoidal signal generator

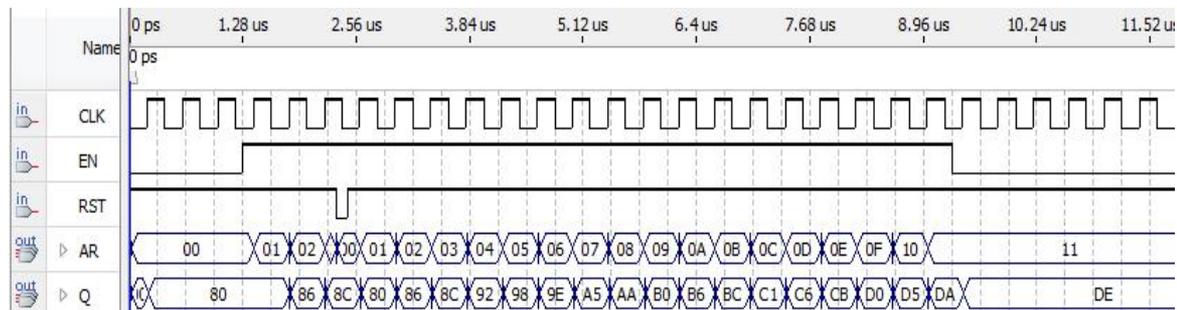


Figure: The circuit simulation waveform

# 6.4.2 Hardware Implementation and Testing of Sinusoidal Signal Generator

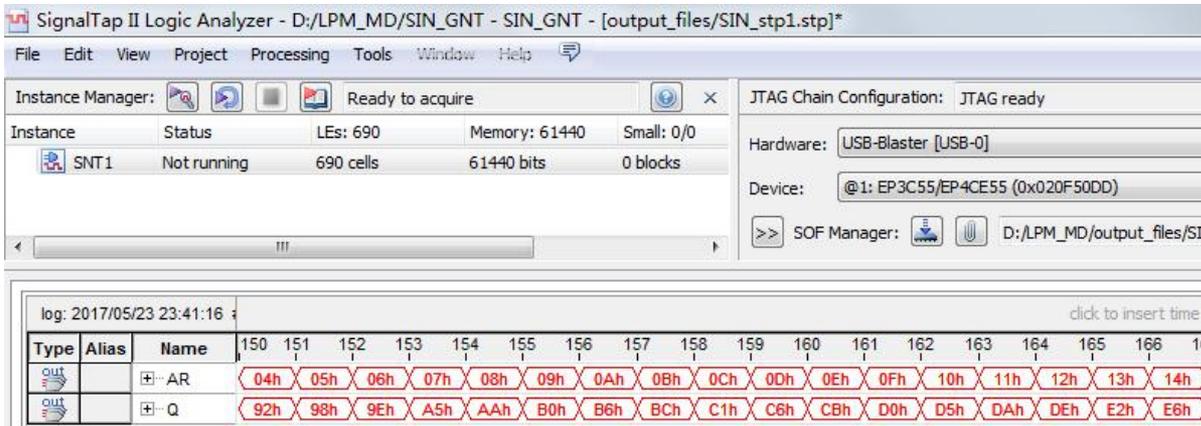


Figure: SignalTap II real-time test interface of sinusoidal signal generator data output

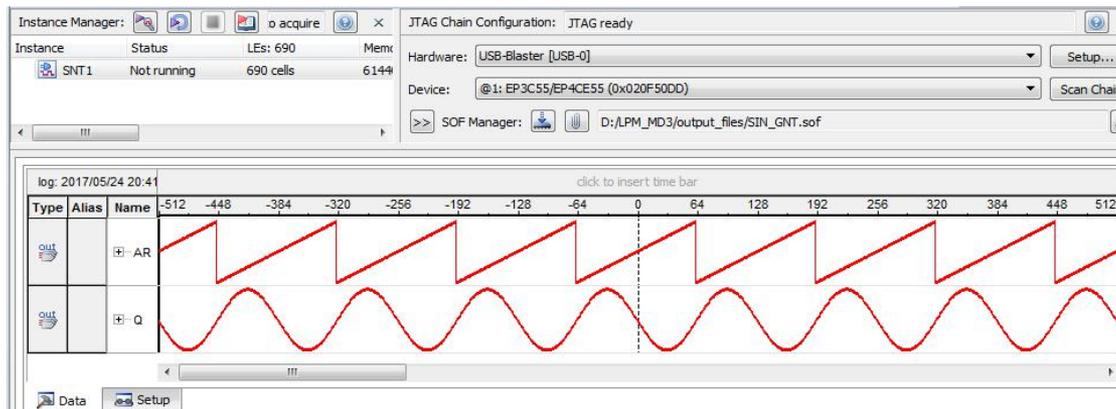


Figure: The waveform display diagram of SignalTap II for sine signal generator

# 6.5 Application of In-System Memory Content Editor

## (1) Open the editing window of in-system memory content editor

The in-system memory content editor of Quartus II reads or writes the data of the operating memory of FPGA via JTAG port, and the read or write process does not affect the operation of the FPGA.

Tool->In-System Memory Content Editor.

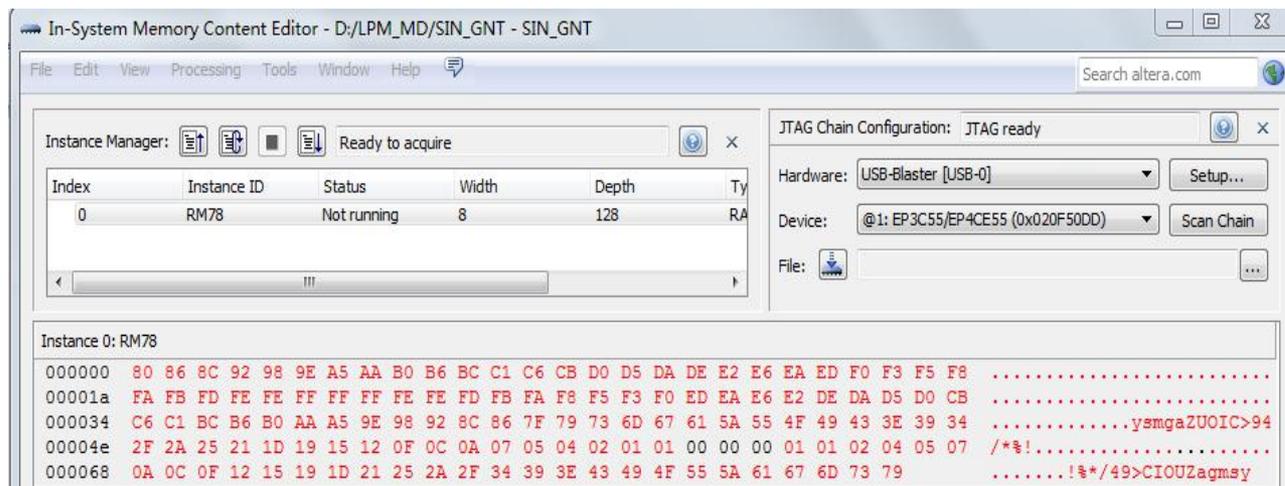


Figure: In-System Memory Content Editor editing window, reading waveform data from the ROM of FPGA

## (2) Read the data of the ROM

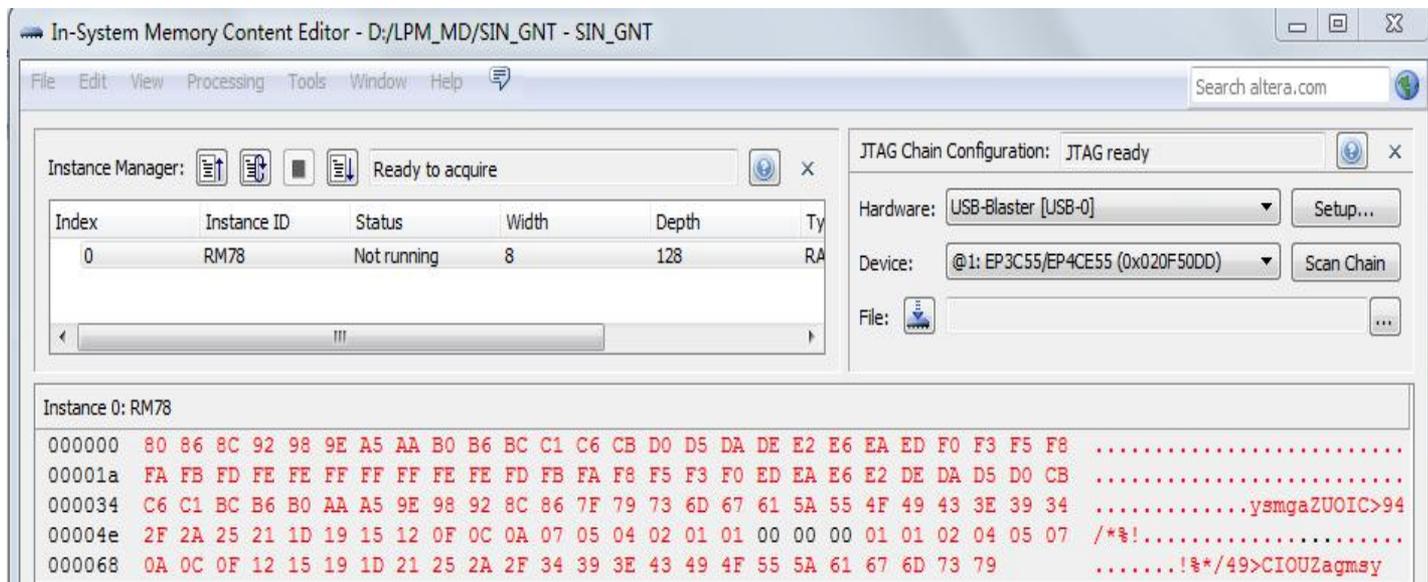


Figure: In-System Memory Content Editor editing window, reading waveform data from the ROM of FPGA

### (3) Write data

```
Instance 0: RM78
000000 11 11 11 11 11 11 11 11 AA B0 B6 BC C1 C6 CB D0 D5 DA DE E2 E6 EA ED F0 F3 F5 F8
00001a FA FB FD FE FE FF FF FF FE FE FD FB FA F8 F5 F3 F0 ED EA E6 E2 DE DA D5 D0 CB
000034 C6 C1 BC B6 B0 AA A5 9E 98 92 8C 86 7F 79 73 6D 67 61 5A 55 4F 49 43 3E 39 34
00004e 2F 2A 25 21 1D 19 15 12 0F 0C 0A 07 05 04 02 01 01 00 00 00 01 01 02 04 05 07
000068 0A 0C 0F 12 15 19 1D 21 25 2A 2F 34 39 3E 43 49 4F 55 5A 61 67 6D 73 79
```

Figure: Here, the edited data is loaded into the ROM in the FPGA

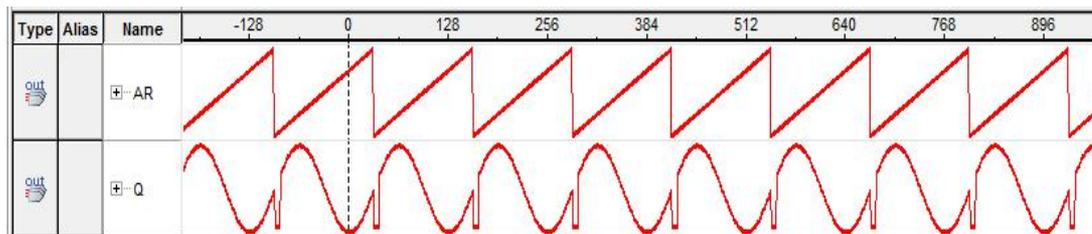


Figure: The data waveform measured by SignalTap II

After modification, choose Write Data to In-System Memory command in the processing menu. Then the edited data can be download to the LPM\_ROM through JTAG port.

#### **(4) The input and output data file**

The data read from the system can be saved as MIF and HEX format file in the computer or “in-system” downloaded to the FPGA, through the command of Export Data to File or Import Data from File in the menu.

# 6.6 Invoke of Embedded PLL of LPM

The Cyclone/II/III/IV and Stratix/II/III/IV FPGA contain high performance PLL, which can be synchronized with the input clock signal. The input clock signal is also severed as the reference. The PLL can thus output one or several synchronized frequency scaling or frequency division on-chip clock.

# 6.6.1 Building Embedded PLL Component


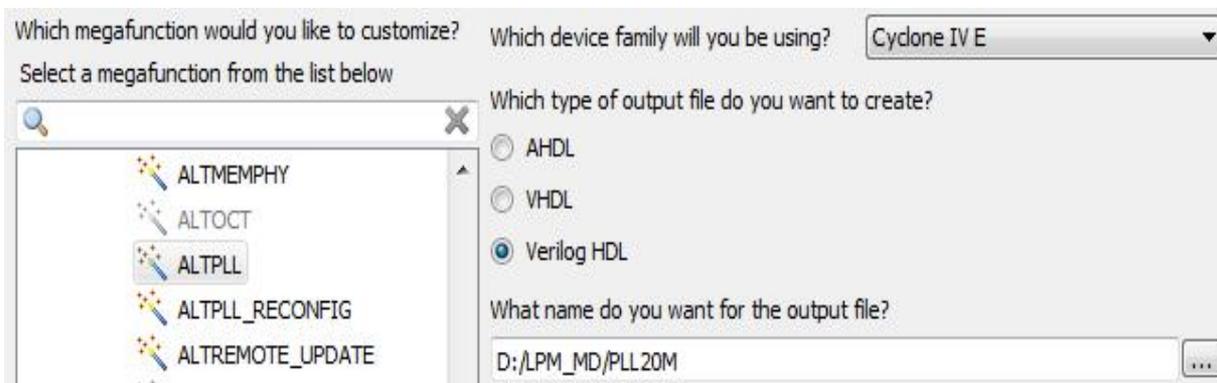


Figure: Choosing phase-locked loop ALTPLL

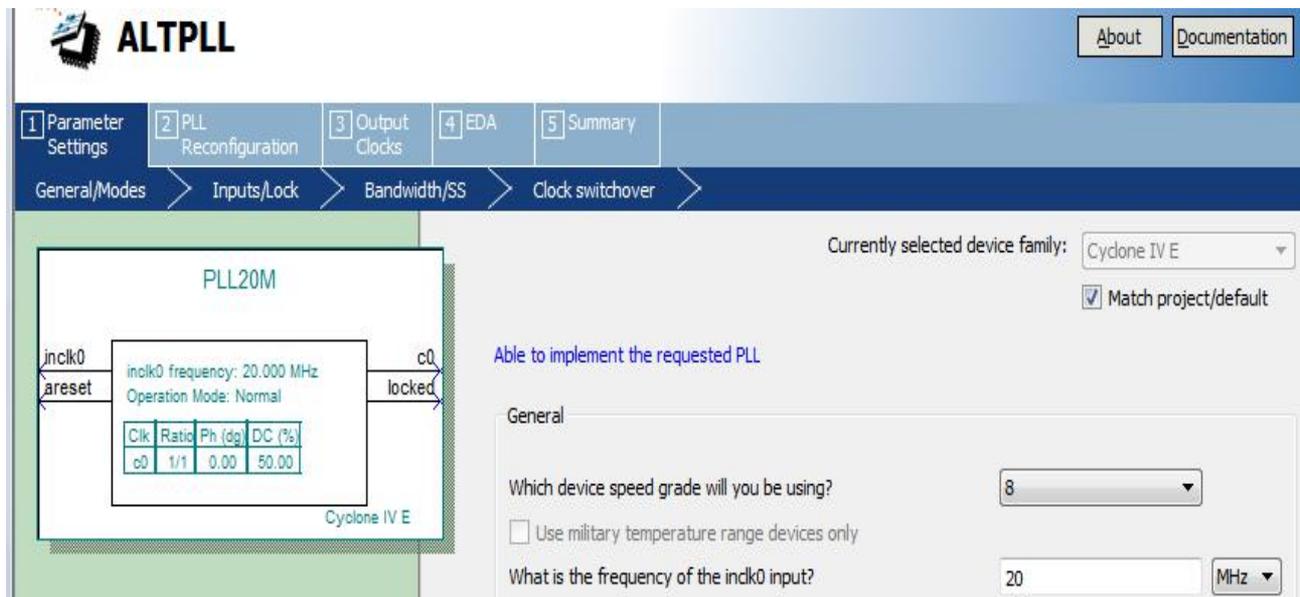

**ALTPLL** [About] [Documentation]

1 Parameter Settings | 2 PLL Reconfiguration | 3 Output Clocks | 4 EDA | 5 Summary

General/Modes > Inputs/Lock > Bandwidth/SS > Clock switchover >

Currently selected device family: Cyclone IV E  
 Match project/default

Able to implement the requested PLL

General

Which device speed grade will you be using? 8

Use military temperature range devices only

What is the frequency of the inclk0 input? 20 MHz

**PLL20M**

inclk0  
areset  
c0  
locked

inclk0 frequency: 20.000 MHz  
 Operation Mode: Normal

Clk	Ratio	Ph (dg)	DC (%)
c0	1/1	0.00	50.00

Cyclone IV E

Figure: Selecting the input reference clock inclk0 to be 20MHz

MegaWizard Plug-In Manager->Create a new custom->I/O->ALTPLL


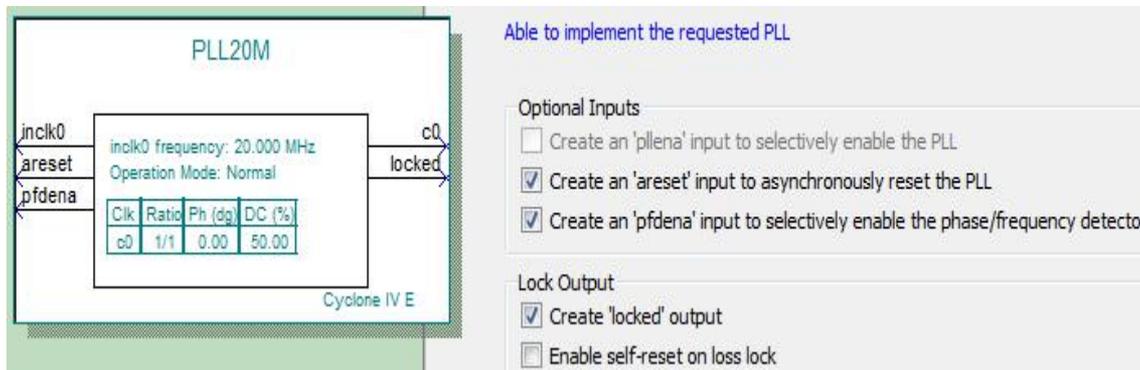


Figure: Selecting the control signal of the PLL

PLL enable: pllena

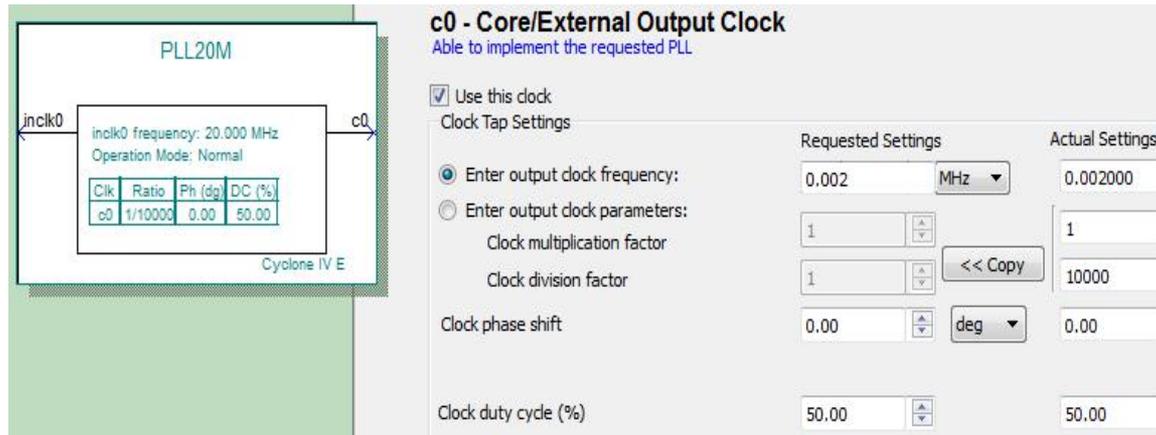asynchronous reset: areset lock output: locked



The image shows a schematic block labeled "PLL20M" and its corresponding configuration window. The schematic block has an input "inclk0" and an output "c0". Inside the block, it specifies "inclk0 frequency: 20.000 MHz" and "Operation Mode: Normal". A table within the block shows the output clock configuration:

Clk	Ratio	Ph (dg)	DC (%)
c0	1/10000	0.00	50.00

The configuration window, titled "c0 - Core/External Output Clock", includes the following settings:

- Use this dock
- Use "Enter output dock frequency:" (selected)
- Requested Settings: 0.002 MHz
- Actual Settings: 0.002000
- Use "Enter output dock parameters:" (unselected)
- Requested Settings: Clock multiplication factor = 1, Clock division factor = 1
- Actual Settings: Clock multiplication factor = 1, Clock division factor = 10000
- Requested Settings: Clock phase shift = 0.00 deg
- Actual Settings: Clock phase shift = 0.00
- Requested Settings: Clock duty cycle (%) = 50.00
- Actual Settings: Clock duty cycle (%) = 50.00

Figure: Selecting the output frequency of c0 to be 0.002MHz

Set up the frequency, phase and duty circle of the output clock



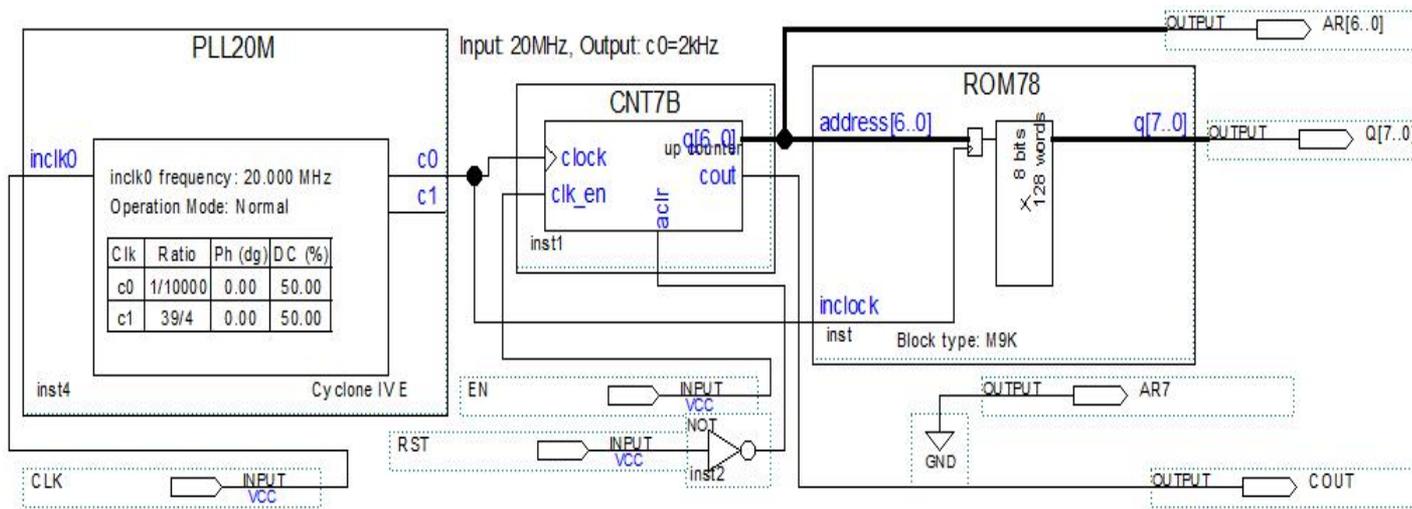


Figure: A sinusoidal signal generator circuit using embedded phase-locked loop as the clock

# 6.7 The Usage of In-System Sources and Probes Editor

SignalTap II and In-System Memory Content Editor can bring great convenience for logic system design, test and debug. However, they also have some disadvantages. For example, SignalTap II (1) occupies a large number of memory units as the data buffer; (2) unidirectionally gather and display the information of hardware system in the operation and can not interact with the system bidirectionally. In-System Memory Content Editor can interact with the system bidirectionally, the target of which is however only confined to memory.

In-System Sources and Probes Editor can overcome the above-mentioned drawback. In particular, the test signal for the system hardware does not have to connect to the I/O port (i.e. all the test signal internally connects to the test system) . All these tasks are realized by the communication through JTAG port of FPGA.

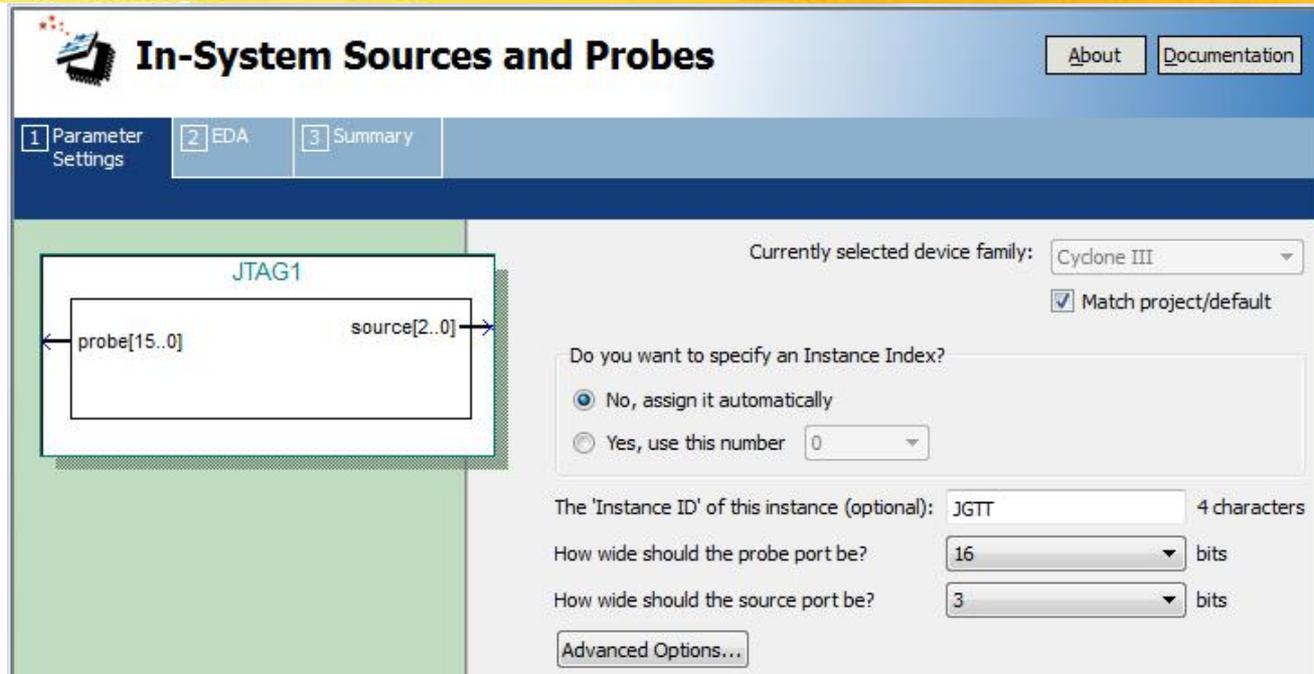


Figure: Setting the parameters for In-System Sources and Probes module

MegaWizard Plug-In Manager->Create a new custom megafunction variation->JTAG-accessible->In System Sources and Probes

The testing port "probe" of the "JTAG1" module is set up to be 16 bits and the signal source is 3 bits.

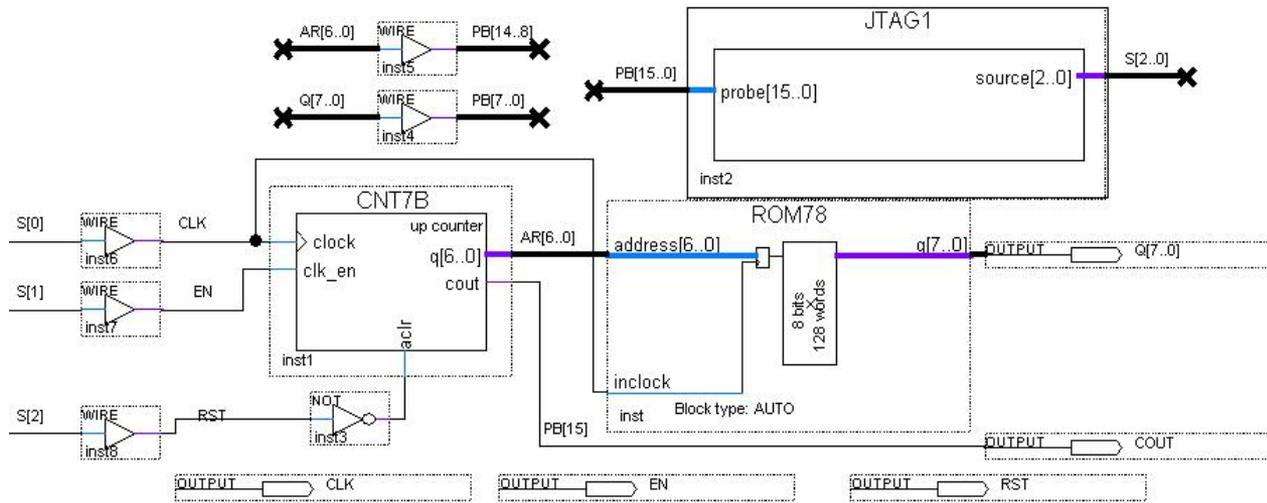


Figure: Adding In-System Sources and Probes testing module in the circuit

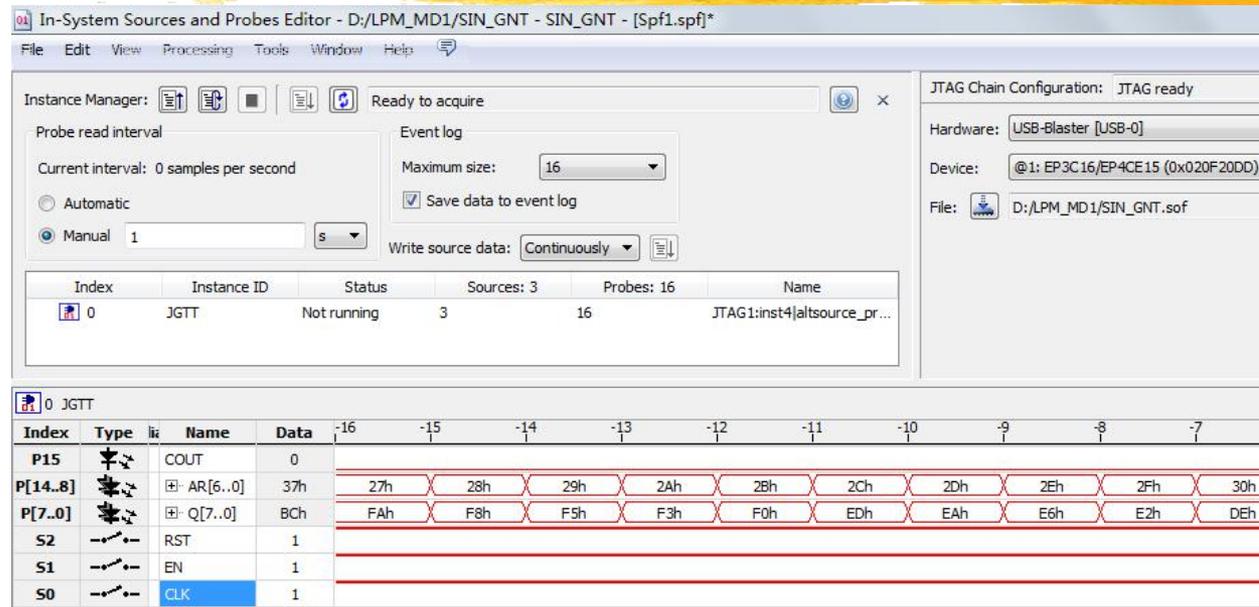


Figure: The testing condition of In-System Sources and Probes Editor

Tool->In-System Sources and Probes Editor

Maximum Size of Event Log refers to the number of sampling period, which is usually 8~32, (most of time is 32)。

S2、S1、S0 are the signals controlling the output of the source, which corresponds to RST、EN、CLK respectively.

# 6.8 Principle and Application of DDS

Direct Digital Synthesizer (DDS) is a frequency synthesis technology, which has high frequency resolution, can achieve fast frequency switching, and can keep the continuous phase in the change. It is easy to realize the numerical control modulation of frequency, phase and amplitude. Therefore, the application of direct digital frequency synthesizer is particularly extensive in the design of frequency source of modern electronic systems and equipment, especially in the field of communication. This section introduces the working principle of DDS and its hardware implementation.

# 6.8.1 Principle of DDS

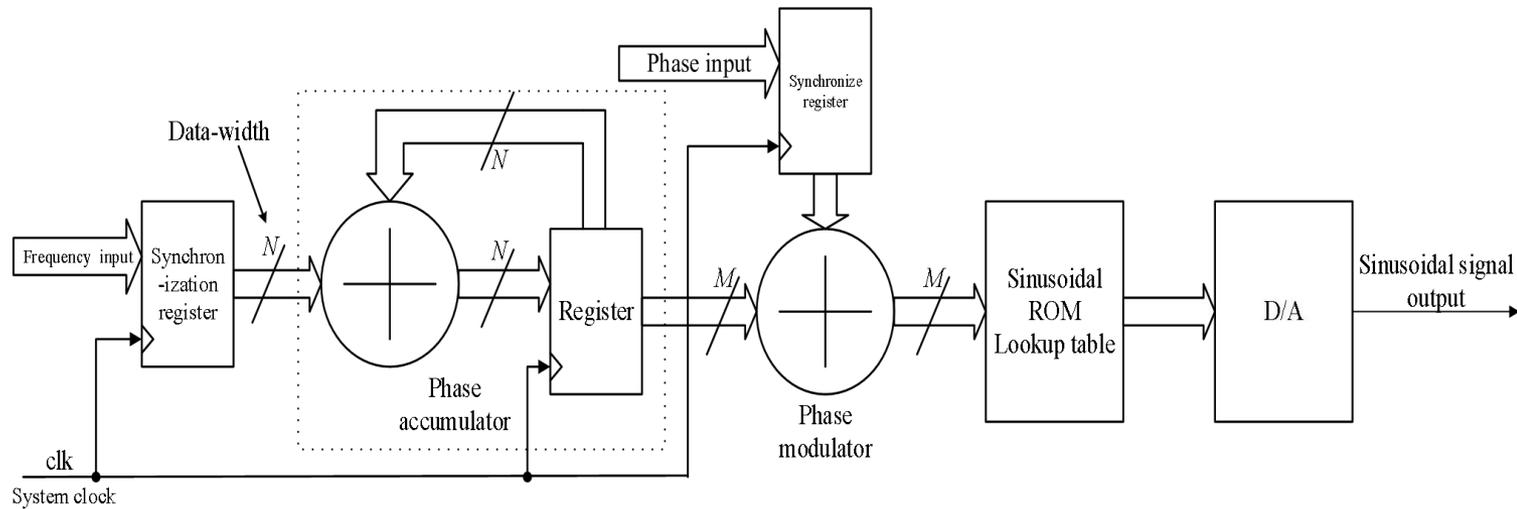


Figure: Basic DDS structure



DDS has the following four features.

(1) Theoretically, the frequency resolution of DDS can get the corresponding resolution accuracy when the bit number  $N$  of phase accumulator is large enough, which is difficult to achieve by traditional methods.

(2) DDS is an open loop system of fully digital structure without feedback link, so its speed is extremely fast, usually in the nanosecond order.

(3) The phase error of DDS mainly depends on the phase characteristics of the clock, and the phase error is small.

(4) The phase of DDS continuously changes, and the signal formed has good frequency spectrum, which cannot be realized by the traditional direct frequency synthesis method.

# 6.8.2 Example of DDS Signal Generator

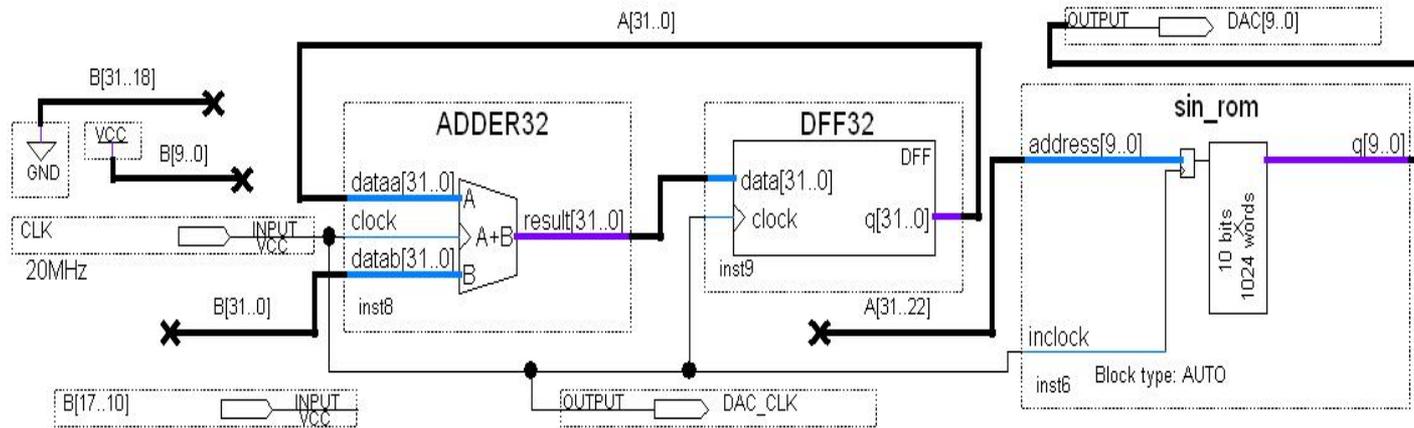


Figure: The top-level schematic diagram of DDS signal generator circuit

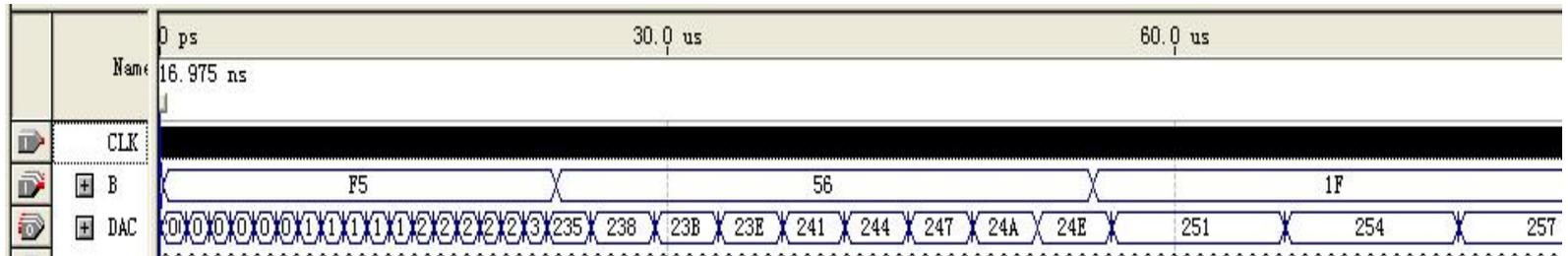


Figure: The simulation waveform of Figure 6-41